
### **TRABALHO 5**

Daniel Salvini e Letícia da Rosa

#### **ALGORITMO**

começa	R2 = B * x
calcula x * x	calcula R1 + R2
R1 = x * x	R1 = R1 + R2
calcula A * R1	calcula R1 + C
R1 = A * R1	R1 = R1 + C
calcula B * x	finaliza

### **DIAGRAMA DE ESTADOS**

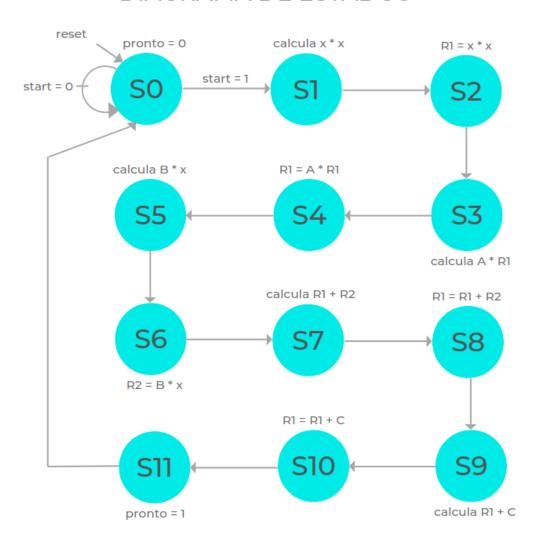

# TABELA DE TRANSIÇÃO DOS ESTADOS

	ENTRADA	ESTADO ATUAL			PRÓXIMO ESTADO					
	START	Q3 <sub>t</sub>	Q2 <sub>t</sub>	Q1 <sub>t</sub>	Q0 <sub>t</sub>	Q3 <sub>t+1</sub>	Q2 <sub>t+1</sub>	Q1 <sub>t+1</sub>	Q0 <sub>t+1</sub>	
SO	0	0	0	0	0	0	0	0	0	S0
SO	1	0	0	0	0	0	0	0	1	S1
S1	X	0	0	0	1	0	0	1	0	S2
S2	Х	0	0	1	0	0	0	1	1	S3
S3	Х	0	0	1	1	0	1	0	0	S4
<b>S</b> 4	×	0	1	0	0	0	1	0	1	S5
S5	×	0	1	0	1	0	1	1	0	S6
S6	×	0	1	1	0	0	1	1	1	S7
<b>S</b> 7	Х	0	1	1	1	1	0	0	0	S8
S8	×	1	0	0	0	1	0	0	1	S9
S9	Х	1	0	0	1	1	0	1	0	S10
S10	X	1	0	1	0	1	0	1	1	S11
S11	×	1	0	1	1	0	0	0	0	S0

# MAPAS DE KARNAUGH DA TRANSIÇÃO DE ESTADOS

START = A Q3 = B

Q2 = C

Q1 = D

Q0 = E

Q0

Q1

	$\overline{\mathrm{D.E}}$	D.E	D.E	$D.\overline{E}$
$\overline{A}.\overline{B}.\overline{C}$	0	0	0	1
$\overline{A}.\overline{B}.C$	1	0	0	1
A.B.C	X	X	X	X
A.B.C	1	0	0	1
A.B.C	1	0	0	1
A.B.C	1	0	0	1
A.B.C	X	X	X	X
A.B.C	1	0	0	1

y = DE' + CE' + BE' + AE'

y = D'E + DE'

Q2

Q3

	$\overline{D}.\overline{E}$	$\overline{D}.E$	D.E	$D.\overline{\overline{E}}$
$\overline{A}.\overline{B}.\overline{C}$	0	0	1	0
$\overline{A}.\overline{B}.C$	1	1	0	1
A.B.C	x	X	X	x
$\overline{A}.B.\overline{C}$	0	0	0	0
A.B.C	0	0	1	0
$A.\overline{B}.C$	1	1	0	1
A.B.C	x	X	X	x
$A.B.\overline{C}$	0	0	0	0

y = CD' + CE' + B'C'DE

y = BD' + BE' + CDE

## TABELA DE SAÍDA

ESTADO					ENT	RADAS	S BO				
Q3 <sub>t</sub>	Q2 <sub>t</sub>	Q1 <sub>t</sub>	Q0 <sub>t</sub>	LX	LH	LL	МО	M1	M2	н	PRONTO
0	0	0	0	1	0	0	00	00	00	0	0
0	0	0	1	0	0	0	00	00	01	1	0
0	0	1	0	0	0	1	00	00	01	1	0
0	0	1	1	0	0	0	01	10	00	1	0
0	1	0	0	0	0	1	01	10	00	1	0
0	1	0	1	0	0	0	10	00	00	1	0
0	1	1	0	0	1	0	10	00	00	1	0
0	1	1	1	0	0	0	00	10	11	0	0
1	0	0	0	0	0	1	00	10	11	0	0
1	0	0	1	0	0	0	11	10	00	0	0
1	0	1	0	0	0	1	11	10	00	0	0
1	0	1	1	0	0	0	00	00	00	0	1

## MAPAS DE KARNAUGH DA LÓGICA DE SAÍDA

LX

	$\overline{C}.\overline{D}$	$\overline{\mathrm{C}}.\mathrm{D}$	C.D	$C.\overline{D}$
$\overline{A}.\overline{B}$	1	0	0	0
Ā.B	0	0	0	0
A.B	X	X	x	X
$A.\overline{B}$	0	0	0	0

y = A'B'C'D'

LH

	$\overline{C}.\overline{D}$	$\overline{\mathrm{C}}.\mathrm{D}$	C.D	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	0	0	0
Ā.B	0	0	0	1
A.B	X	X	x	X
$A.\overline{B}$	0	0	0	0

y = BCD'

LL

	$\overline{C}.\overline{D}$	$\overline{\mathrm{C}}.\mathrm{D}$	C.D	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	0	0	1
$\overline{A}$ .B	1	0	0	0
A.B	X	X	x	X
$A.\overline{B}$	1	0	0	1

y = AD' + B'CD' + BC'D'

Н

	$\overline{C}.\overline{D}$	$\overline{\mathrm{C}}.\mathrm{D}$	C.D	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	1	1	1
$\overline{A}$ .B	1	1	0	1
A.B	X	X	x	x
$A.\overline{B}$	0	0	0	0

y = BD' + A'B'C + A'C'D

**PRONTO** 

y = ACD

Q3 = A Q2 = B Q1 = C Q0 = D

#### **M00**

#### 

y = BC'D + BCD' + AC'D + ACD'

#### M01

	$\overline{C}.\overline{D}$	$\overline{\mathrm{C}}.\mathrm{D}$	C.D	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	0	1	0
$\overline{A}$ .B	1	0	0	0
A.B	X	X	x	X
$A.\overline{B}$	0	1	0	1

y = BC'D' + AC'D + ACD' + A'B'CD

#### **M10**

#### 

y = AC' + AD' + A'CD + BC'D'

**M11** 

	$\overline{C}.\overline{D}$	$\overline{C}.D$	C.D	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	0	0	0
$\overline{A}$ .B	0	0	0	0
A.B	X	X	X	X
$A.\overline{B}$	0	0	0	0

y = 0

#### **M20**

	$\overline{C}.\overline{D}$	$\overline{C}.D$	C.D	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	0	0	0
$\overline{A}$ .B	0	0	1	0
A.B	X	X	x	X
$A.\overline{B}$	1	0	0	0

y = BCD + AC'D'

**M21** 

	$\overline{C}.\overline{D}$	$\overline{\mathrm{C}}.\mathrm{D}$	C.D	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	1	0	1
$\overline{A}$ .B	0	0	1	0
A.B	X	X	X	X
$A.\overline{B}$	1	0	0	0

y = BCD + AC'D' + A'B'C'D + A'B'CD'